

國立臺北科技大學

102 學年第一學期電機系博士班資格考試

電力電子學試題


第一頁 共二頁

--	--	--	--	--	--	--	--


注意事項：

1. 本試題共十題，配分共 100 分。
2. 請按順序標明題號作答，不必抄題。
3. 全部答案均須答在試卷答案欄內，否則不予計分。
4. 考試時間：二小時。
5. 可使用計算器。

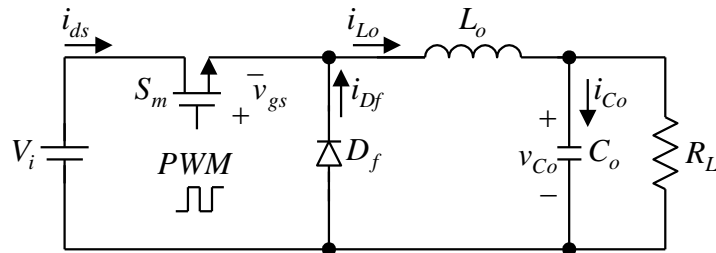1. (10%) If the following converter operates in CCM, please sketch in turn the waveforms of PWM(= v_{gs}), i_{ds} , i_{Df} , i_{Lo} , i_{Co} , v_{Co} .



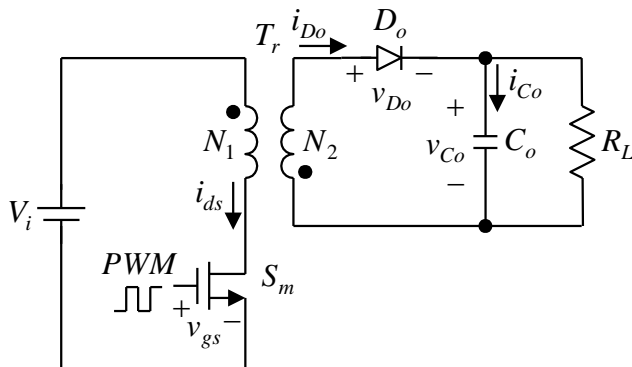2. (10%) If the following converter operates in CCM, please sketch in turn the waveforms of PWM(= v_{gs}), i_{ds} , i_{Do} , v_{Do} , i_{Co} , v_{Co} .



3. (10%) For a buck converter to be considered:
 - a) Please plot $I_{LB} / I_{LB,\max}$ versus D under a fixed value of V_o , where $I_{LB,\max} = \frac{T_s V_o}{2L}$.
 - b) Please plot $I_{LB} / I_{LB,\max}$ versus D under a fixed value of V_i , where $I_{LB,\max} = \frac{T_s V_i}{8L}$.
4. (10%) For a boost converter operating in DCM, please plot the corresponding operating area based on the curve of duty cycle versus load current with the BCM line used as a boundary.
5. (10%) A buck-boost converter operates in CCM. If $V_i = 8 \sim 40\text{V}$, $V_o = 15\text{V}$, $f_s = 20\text{kHz}$, $P_o \geq 2\text{W}$ and all the elements are ideal, then please find L_{\min} .
6. (10%) Under the condition of no power loss, please prove that for the AC-DC converter with the power factor equal to 1, the instantaneous output power has an AC component of double the line frequency.
7. (10%) Please find and prove the voltage conversion ratio of the current-fed push-pull converter operating in CCM.
8. (10%) Please give an illustration for the reason why the peak current mode control needs the slope compensation.
9. (10%) Please plot B-H curves for the following individual magnetic devices:
 - 1) for the output inductor of the buck converter operating in DCM.
 - 2) for the output inductor of the buck converter operating in CCM.
 - 3) for the transformer of the forward converter operating in CCM.
 - 4) for the transformer of the flyback converter operating in DCM.
 - 5) for the transformer of the flyback converter operating in CCM.
10. (10%) Please find the effect of the blanking time on the output voltage of the DC-AC inverter, if the load is inductive. Speaking lucidly, plot the relationship between the ideal output voltage and the actual output voltage, based on the output current.