國立臺北科技大學

九十七學年第二學期電機系博士班資格考試

變頻器試題

第一頁 共一頁



注意事項:

- 1. 本試題共【6】題,配分共100分。
- 2. 請按順序標明題號作答,不必抄題。
- 3. 全部答案均須答在試卷答案欄內,否則不予計分。
- 4. 考試時間:二小時。
- Fig. 1 shows the block diagram of vector-controlled induction motor drives. Please highlight the error in Fig. 1. (20%)

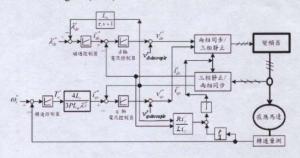


Fig. 1 Block diagram of vector-controlled induction motor drives

- 2. Given the sampled modulating signals at two consecutive time sampled instants are $M \sin(\omega t_k)$ and $M \sin(\omega t_{k+1})$, and the triangular carrier period is T, Please derive the related pulse width for PWM control. (15%)
- What is two-phase modulation PWM? (5%) What is Universal Space Vector Modulation? (10%)
- 4. Draw the waveforms of common-mode voltage for three-phase inverter for the switching

states (100), (110) and (000). (10%) (Assuming the DC link voltage = V_{DC})

- Illustrate two methods for reducing or blocking the bearing current for three-phase inverter-controller induction motor drives. (10%) And show how these methods can achieve that. (10%)
- 6. For the induction motor model shown in the equation:

$$\vec{v}_s^e = \vec{i}_s^e R_s + j\omega \vec{\lambda}_s^e + p\vec{\lambda}_s^e$$

$$0 = \vec{l}_r^e R_r + j(\omega - \omega_r) \vec{\lambda}_r^e + p \vec{\lambda}_r^e$$
 and with rotor flux oriented control

$$\vec{\lambda}_s^e = L_s \vec{i}_s^e + L_m \vec{i}_r^e$$

$$\vec{\lambda}_r^e = L_m \vec{i}_s^e + L_r \vec{i}_r^e$$

Derive the (1). Slip frequency, and (2). Voltage model of the flux estimator (20%).