

# 國立臺北科技大學

103 學年第一學期電機系博士班資格考試

## 電力電子學試題


第一頁 共三頁

--	--	--	--	--	--	--	--


### 注意事項：

1. 本試題共六題，配分共 100 分。
2. 請按順序標明題號作答，不必抄題。
3. 全部答案均須答在試卷答案欄內，否則不予計分。
4. 考試時間：二小時。
5. 可使用計算器。

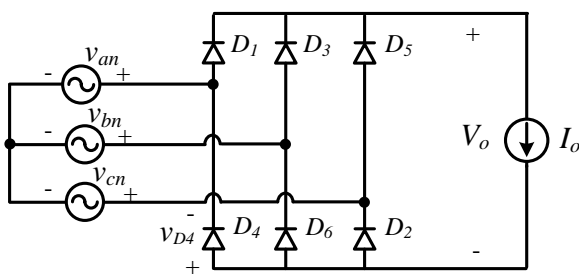1. (15%) Figure 1(a) shows an ideal three-phase AC-DC rectifier, load current  $I_o$  is constant. Sketch voltage of the diode  $D_4$  (at least one period), give your reasoning for the result. The three-phase voltage and line voltages are shown in Fig. 1(b) for your reference.



(a)

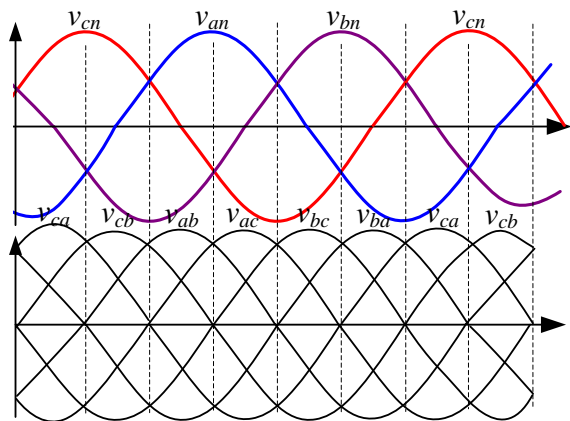

(b)

Fig. 1

2. (15%) Figure 2 shows the voltage and current waveform of a power supply, find its power factor?

(Hint: Fourier series expression of  $i(t) = \frac{4I}{\pi} \sin(\omega t) + \frac{4I}{3\pi} \sin(3\omega t) + \frac{4I}{5\pi} \sin(5\omega t) + \dots$ )

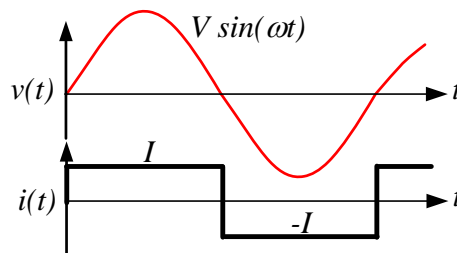


Fig. 2

3. (15%) Figure 3 shows a buck converter,  $V_s$  is input,  $V_o$  is output,  $T$  is the switching period,  $D$  is the duty,  $C$  is very large so  $V_o$  can be assumed to be a constant. All the components are ideal. If the circuit is running at steady state and at the boundary between continuous and discontinuous conduction mode, find  $I_o$  and express it in terms of  $V_s$ ,  $L$ ,  $D$ , and  $T$ ?

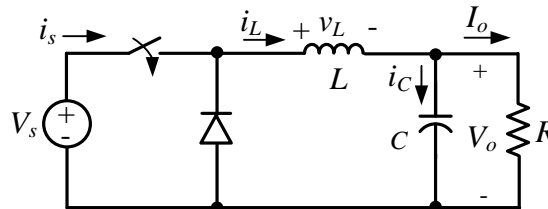


Fig. 3

4. (15%) Figure 4 shows a three-phase DC-AC Inverter, input power source is  $V_i$ ,  $n$  is the neutral point. If switches  $S_1$ ,  $S_2$ , and  $S_6$  are closed (turn on), what is the motor phase voltage  $V_{An}$ ,  $V_{Bn}$ ,  $V_{Cn} = ?$

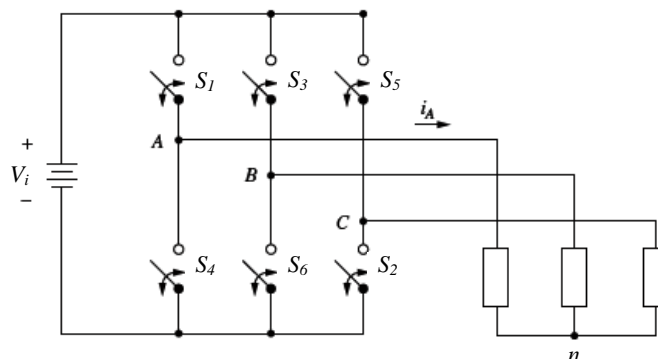


Fig. 4

5. (20%) Figure 5(a) shows a SEPIC Converter. All the components are ideal, and the circuit is running at steady state and continuous conduction mode.  $C1$  is very large so  $v_{C1}$  can be assumed to be a constant. Derive  $V_o/V_s = ?$  If the  $i_{L1}$  and  $i_{L2}$  wave forms are shown in Fig 5(b), sketch the corresponding  $i_{C1}$ ,  $i_{sw}$  and  $i_D$  waveforms?

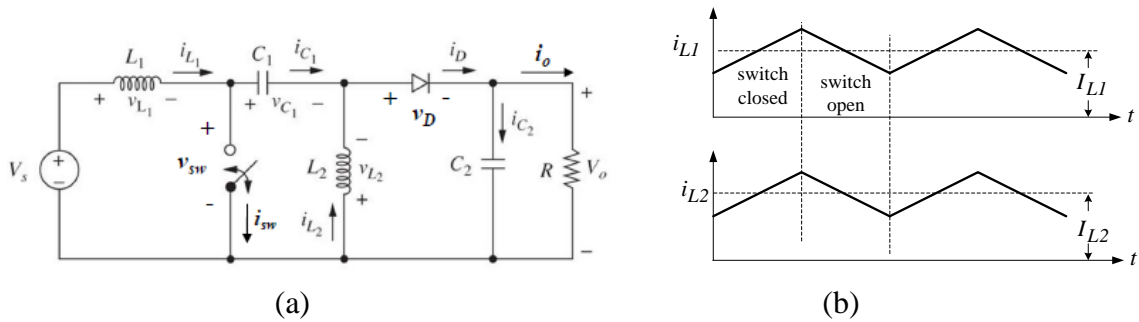


Fig. 5

6. (15%) Figure 6(a) shows a DC-DC Converter, transformer is already expressed in equivalent circuit,  $L_m$  is the excitation inductance, core is completely de-magnetized at the end of each period.  $V_s=150V$ , output voltage is  $V_o$ , output current is  $I_o$ ,  $T$  is the switching period, and  $N1:N2=10:1$ ,  $N1:N3=1:1$ . If  $v_1 \cdot i_m$  and  $i_L$  waveforms are shown in Fig. 6(b), find and sketch  $i_1$  and  $v_{sw}$  waveforms?

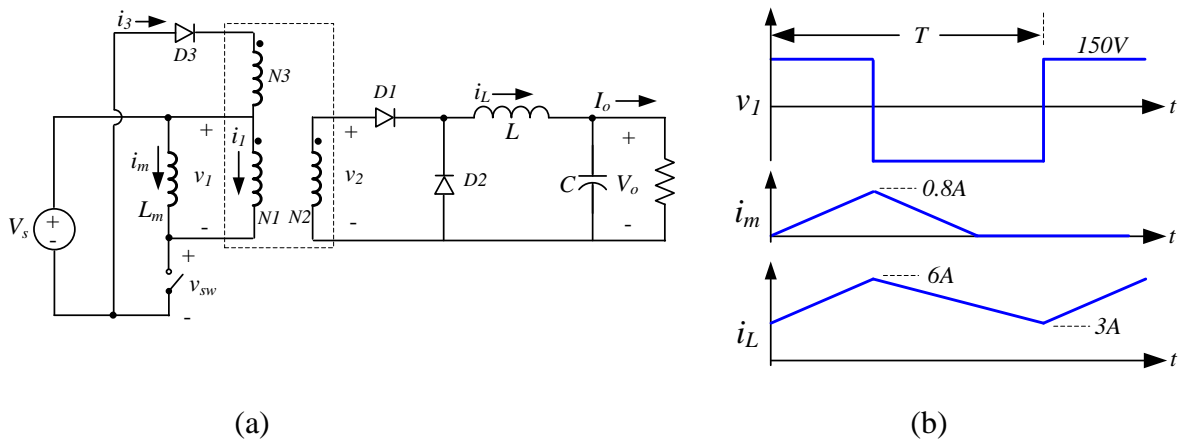


Fig. 6